

---

## Table of Contents

Question 1 .....	1
question 2 .....	7
Question 3 .....	13
Question 4 .....	21

## Question 1

$$V_i = V_{in}$$

$$G_1(V_2 - V_1) + C\left(\frac{d(V_2 - V_1)}{dt}\right) + G_2V_2 - I_L = 0$$

$$V_2 - V_3 - L\frac{dI_L}{dt} = 0$$

$$-I_L + G_3V_3 = 0$$

$$V_4 - \alpha I_3 = 0$$

$$G_3V_3 - I_3 = 0$$

$$G_4(V_O - V_4) + G_OV_O = 0$$

in frequency domain

$$V_i = V_{in}$$

$$G_1(V_2 - V_1) + C(j\omega(V_2 - V_1)) + G_2V_2 - I_L = 0$$

$$V_2 - V_3 - L(j\omega)I_L = 0$$

$$-I_L + G_3V_3 = 0$$

$$V_4 - \alpha I_3 = 0$$

$$G_3V_3 - I_3 = 0$$

$$G_4(V_O - V_4) + G_OV_O = 0$$

```
%variables [v1 v2 v3 v4 v5 Iin IL]
close all
clear
```

```
g1=1;
g2=0.5;
g3=.1;
g4=10;
g5=1e-3;
a=100;
c=0.25;
l=0.2;
```

---

```
% G matrix
G=[1,0,0,0,0,0,0;
   -g2,g1+g2,-1,0,0,0,0;
   0,1,0,-1,0,0,0;
   0,0,-1,g3,0,0,0;
   0,0,0,0,-a,1,0;
   0,0,0,g3,-1,0,0;
   0,0,0,0,0,-g4,g4+g5]

% C matrix
C=[0,0,0,0,0,0,0;
   -c,c,0,0,0,0,0;
   0,0,-1,0,0,0,0;
   0,0,0,0,0,0,0;
   0,0,0,0,0,0,0;
   0,0,0,0,0,0,0;
   0,0,0,0,0,0,0]

q=[];
w=[];

% DC Sweep from -10 to 10
for vin=-10:10
    %F Vector
    F=[vin;0;0;0;0;0;0];
    V=G\F;
    q=[q,V(4)];
    w=[w,V(7)];
end
figure(1)
plot (-10:10,q)
title('Voltage at V3 vs Vin for Vin =-10 to 10 Vdc')
xlabel('Vin (V)')
ylabel('Voltage at V3 (V)')

figure(2)
plot (-10:10,w)
title('Vout vs. Vin for Vin =-10 to 10 Vdc')
xlabel('Vin (V)')
ylabel('Vout (V)')

q=[];
w=[];
vin=1;
for z=1:1000
    F=[vin;0;0;0;0;0;0];
    V=(G+z*1j*C)\F;
```

---

---

```

        w=[w,V(7)];
    end

    figure(3)
    semilogx(1:1000,abs(w))
    title('V0 vs. frequency with 1V amplitude')
    xlabel('Frequency (rad/s)')
    ylabel('Vout (V)')

    figure(4)
    semilogx(1:1000,20*log10(abs(w)))
    title('V0 vs. frequency with 1V amplitude')
    xlabel('Frequency (rad/s)')
    ylabel('Vout (dB)')

    w=[];
    for z=1:1000
        c=0.25+0.05*randn();
        F=[vin;0;0;0;0;0;0;0];
        C= [0,0,0,0,0,0,0,0;
            -c,c,0,0,0,0,0,0;
            0,0,-1,0,0,0,0,0;
            0,0,0,0,0,0,0,0;
            0,0,0,0,0,0,0,0;
            0,0,0,0,0,0,0,0;
            0,0,0,0,0,0,0,0];
        V=(G+pi*1j*C)\F;
        w=[w,V(7)];
    end

    figure(5)
    histogram(20*log10(sqrt(real(w).^2+imag(w).^2)))
    title('Histogram of gain')
    xlabel('Values of gain (dB)')
    ylabel('count')

    G =

        1.0000         0         0         0         0         0         0
       -0.5000     1.5000    -1.0000         0         0         0         0
         0         1.0000         0    -1.0000         0         0         0
         0         0    -1.0000     0.1000         0         0         0
         0         0         0         0   -100.0000     1.0000         0
         0         0         0     0.1000    -1.0000         0         0
         0         0         0         0         0    -10.0000    10.0010

    C =


         0         0         0         0         0         0         0



```



---

---

-0.2500	0.2500	0	0	0	0	0
0	0	-0.2000	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0

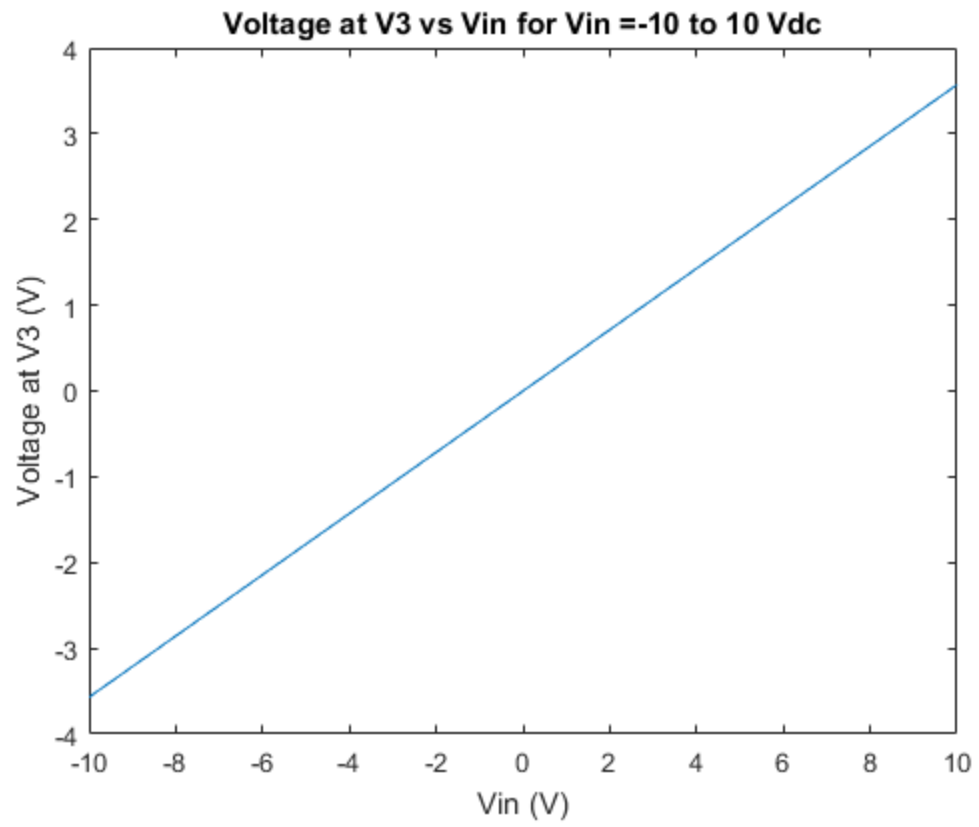

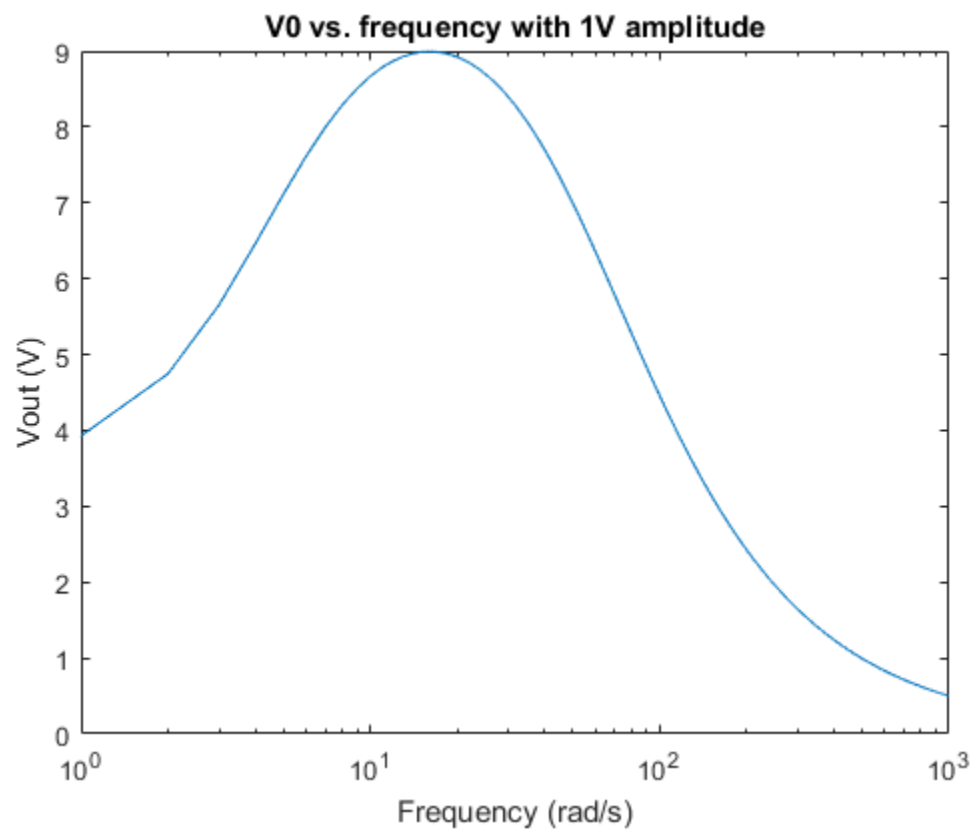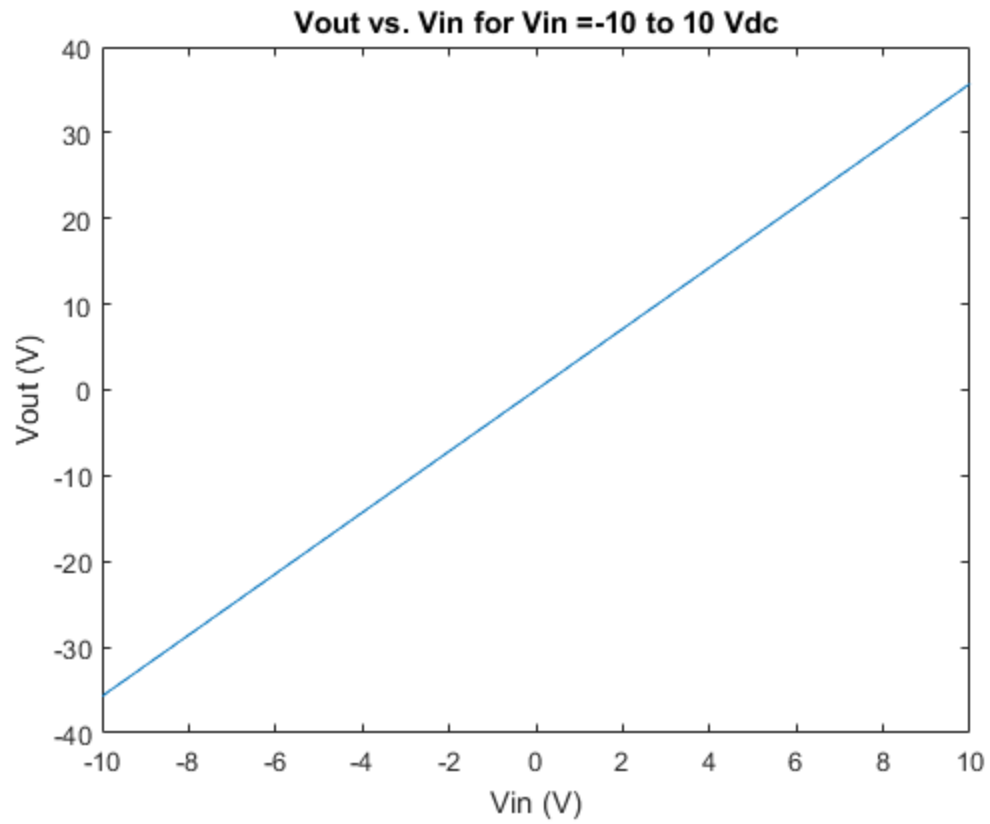

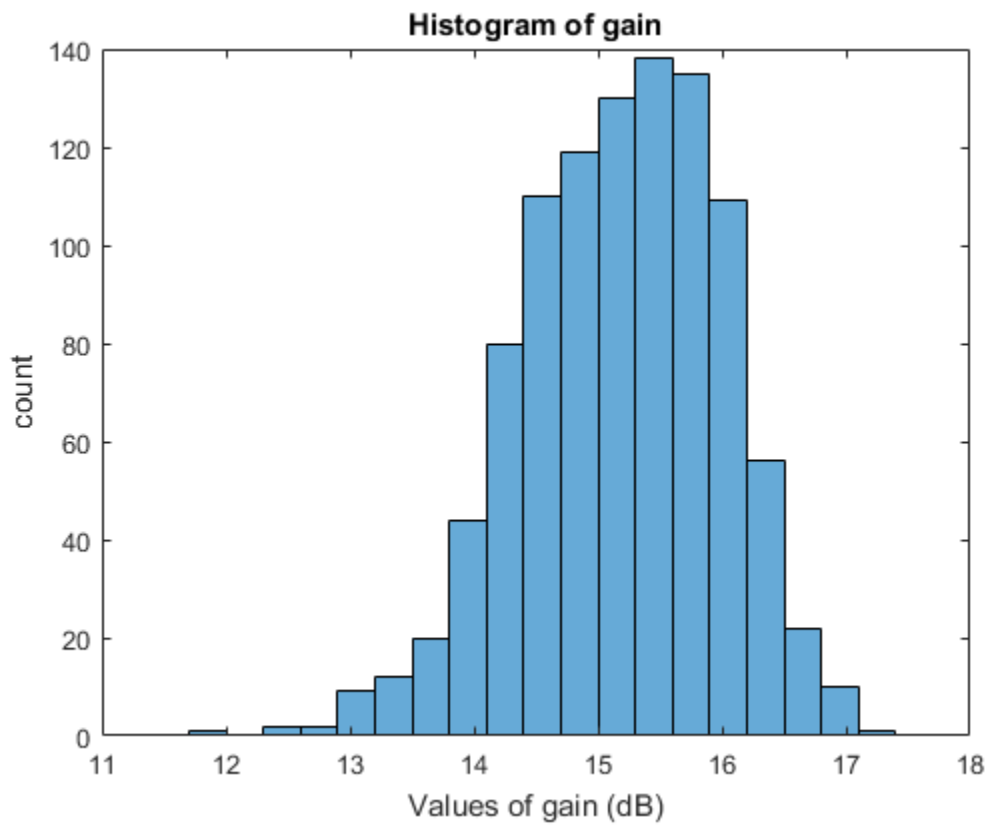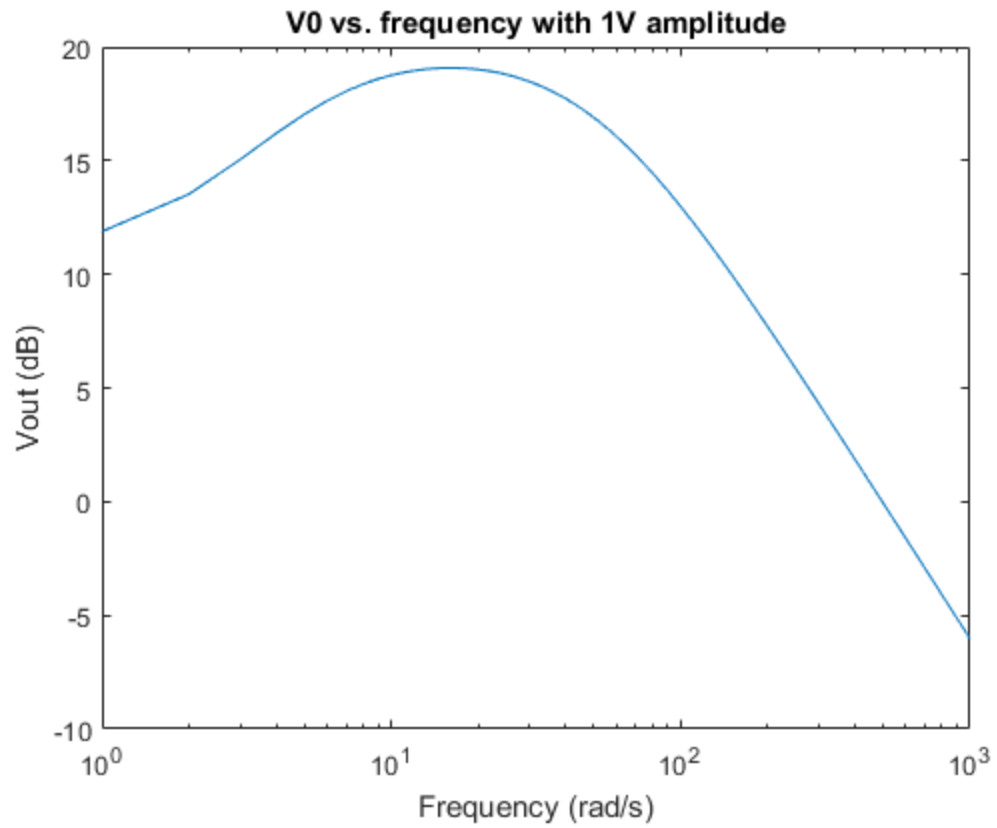

---

## question 2

```
% This is an amplifier circuit. it has a bandpass response due to the
% capacitor and inductor. The resistor parallel to the capacitor
% limits the
% low frequency filtering, so there will be less than a 1st order drop
% off
% for low frequency components. The high frequency components will
% experience first order drop off due to the inductor

% Create the voltage step (F1)
t = linspace(0,1,1000);
vin=1;
F1=0;
for i=1:31
    F1(i,1:7)=[0,0,0,0,0,0,0];
end
for i=32:1000
    F1(i,1:7)=[vin;0;0;0;0;0;0];
end

v1=0;
dt=0.001;
% voltage step output
v1(1:7,1)=(C/dt+G)^-1 *(F1(1,:))';
for i=2:1000
    v1(:,i)=(C/dt+G)^-1 *(C*v1(:,i-1)/dt+F1(i,:))';
end

figure(6)

plot(t,v1(7,:))
hold on
plot(t,F1(:,1))
legend('Vout','input step')
title('DC step response')
xlabel('Time (s)')
ylabel('Voltage (V)')

% create the sin input function
v2=0;
t = linspace(0,1,1000);
f=1/.03;
F2=0;
for i=1:1000
    F2(i,1:7)=[sin(2*pi*f*t(i)),0,0,0,0,0,0];
end

% sin output
v2(1:7,1)=(C/dt+G)^-1 *(F2(1,:))';
for i=2:1000
```

---

```

        v2(:,i)=(C/dt+G)^-1 *(C*v2(:,i-1)/dt+F2(i,:));
    end

    figure(7)
    plot(t,v2(7,:))
    hold on
    plot(t,F2(:,1))
    legend('Vout','input signal')
    title('DC sin responce')
    xlabel('Time (s)')
    ylabel('Voltage (V)')

%guassian function

v3=0;
t = linspace(0,1,1000);
f=1/.03;
F3=0;
for i=1:1000
    F3(i,1:7)=[exp(-1/2*((t(i)-0.06)/0.03)^2),0,0,0,0,0,0];
end

%guassian output
v3(1:7,1)=(C/dt+G)^-1 *(F3(1,:));
for i=2:1000
    v3(:,i)=(C/dt+G)^-1 *(C*v3(:,i-1)/dt+F3(i,:));
end

figure(8)
plot(t,v3(7,:))
hold on
plot(t,F3(:,1))
legend('Vout','input signal')
title('DC Guassian responce')
xlabel('Time (s)')
ylabel('Voltage (V)')

%guassian output larger timestep
dt=0.001;
t = linspace(0,1,100);
v4(1:7,1)=(C/dt+G)^-1 *(F3(1,:));
for i=2:100
    v4(:,i)=(C/dt+G)^-1 *(C*v3(:,i-1)/dt+F3(i,:));
end

figure(9)
plot(t,v4(7,:))
hold on
t = linspace(0,1,1000);
plot(t,F3(:,1))
legend('Vout','input signal')

```

---



---

```

title('DC Guassian responce')
xlabel('Time (s)')
ylabel('Voltage (V)')

figure(10)
semilogy(linspace(-500,500,1000),fftshift(abs(fft(v1(7,:)))))
hold on
semilogy(linspace(-500,500,1000),fftshift(abs(fft(F1(:,1)))))
legend('Vout','input signal')
title('DC Step Fourier Transform')
xlabel('Frequency(rad/s)')
ylabel('Voltage (V)')



figure(11)
semilogy(linspace(-500,500,1000),fftshift(abs(fft(v2(7,:)))))
hold on
semilogy(linspace(-500,500,1000),fftshift(abs(fft(F2(:,1)))))
legend('Vout','input signal')
title('Sin Fourier Transform')
xlabel('Frequency (rad/s)')
ylabel('Voltage (V)')



figure(12)
semilogy(linspace(-500,500,1000),fftshift(abs(fft(v3(7,:)))))
hold on
semilogy(linspace(-500,500,1000),fftshift(abs(fft(F3(:,1)))))
title('Guassian Fourier Transform')
legend('Vout','input signal')
xlabel('Frequency (rad/s)')
ylabel('Voltage (V)')



% As we can see in figure 9, when the time step is enlarged the
% simulation
% behaves unexpectedly. The guassian peak becaomes very delayed in
% time on
% the output, and much wider than expected.


```

---

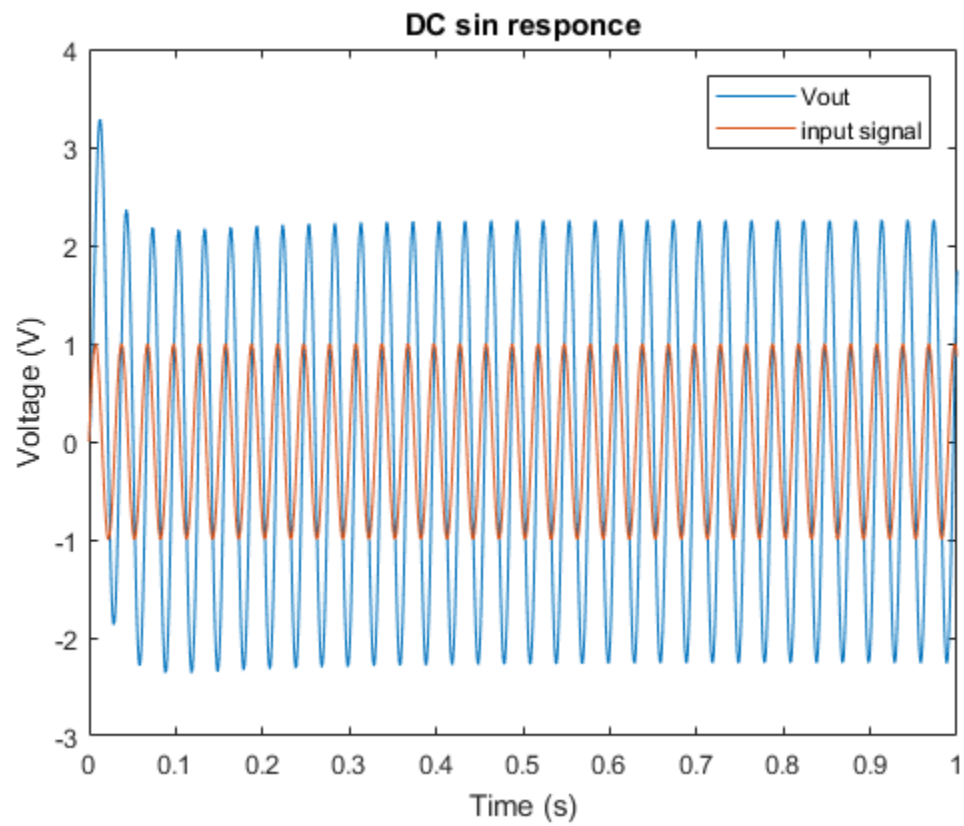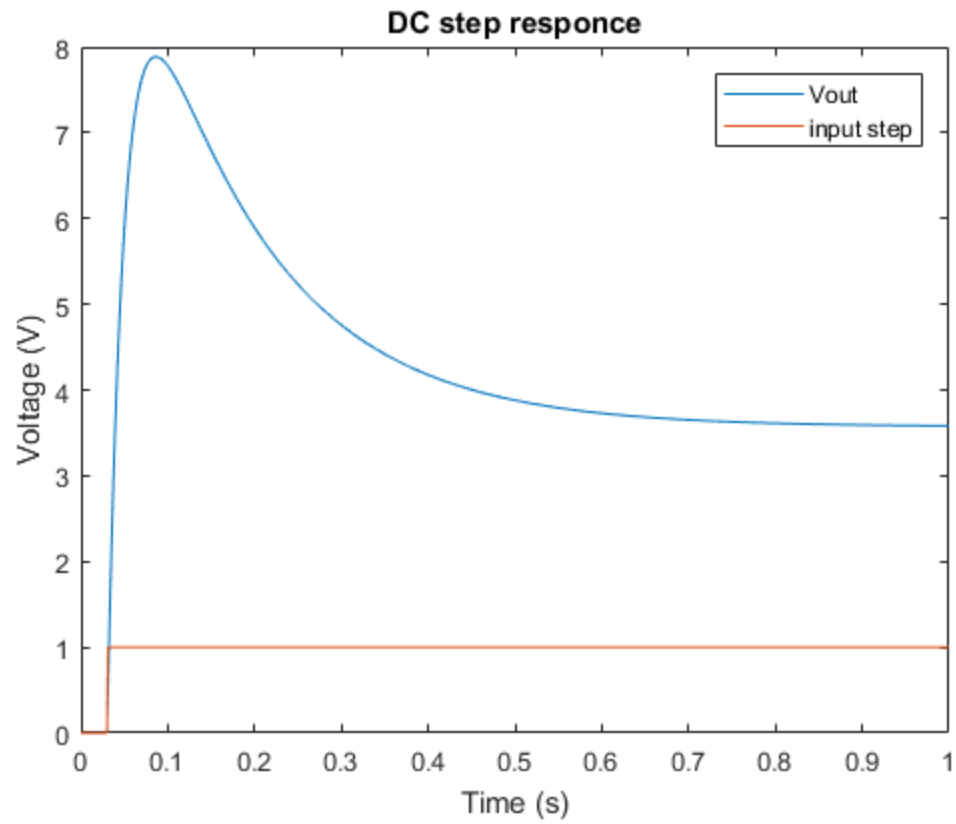

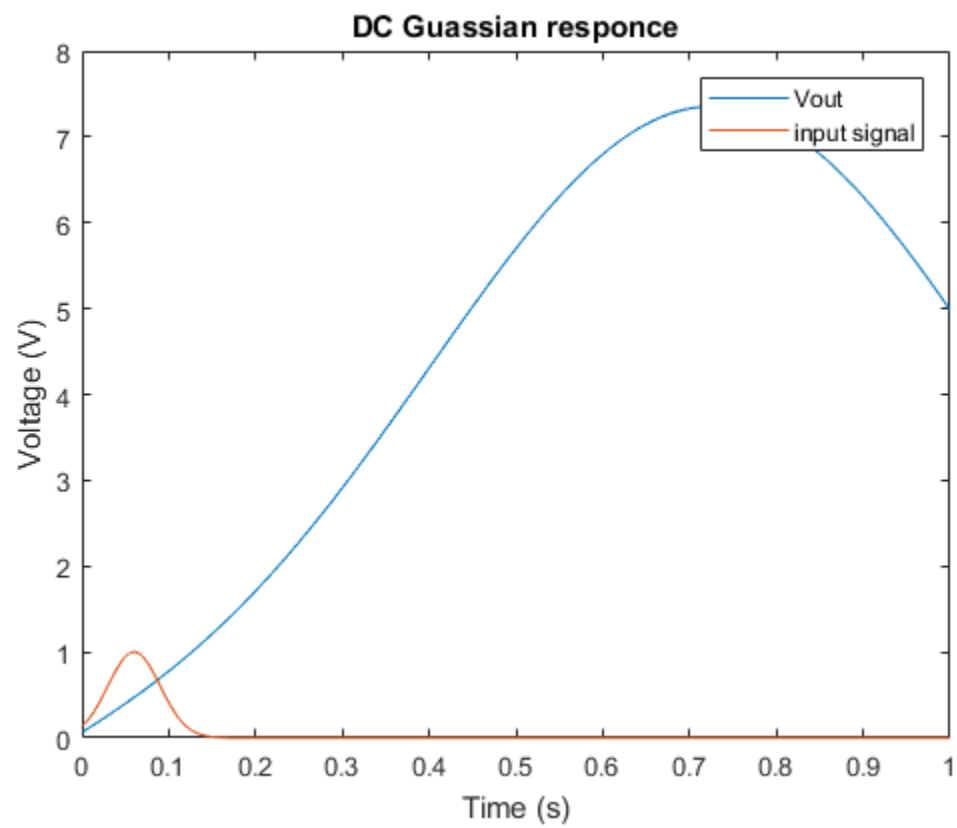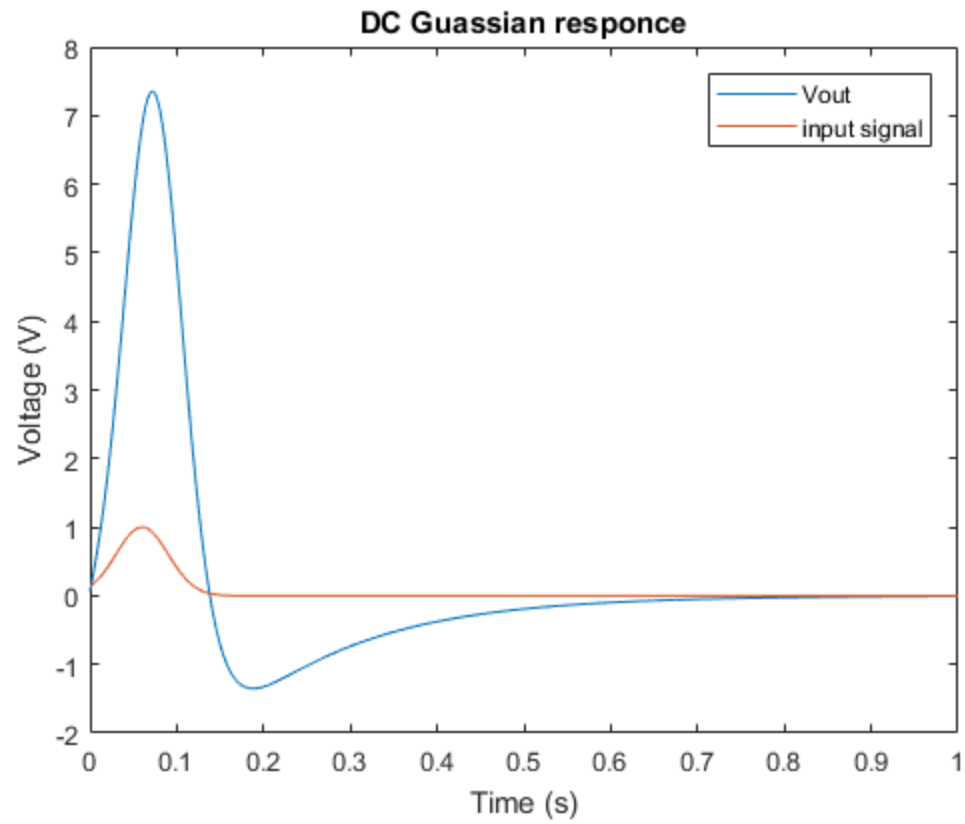

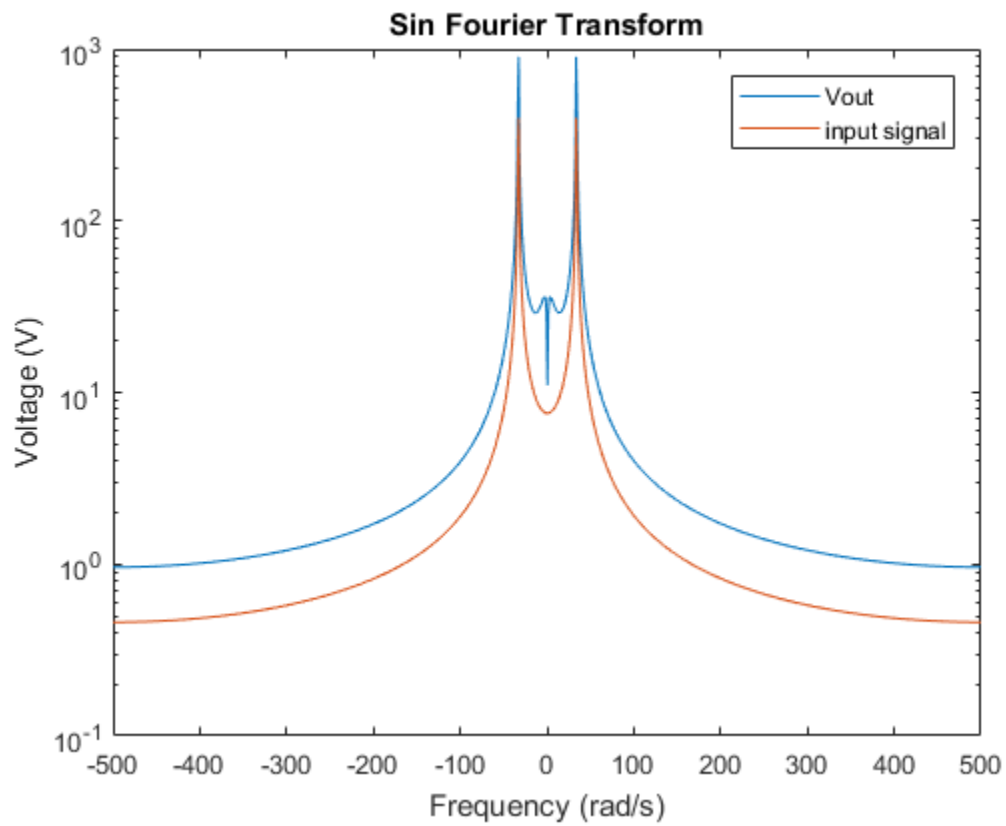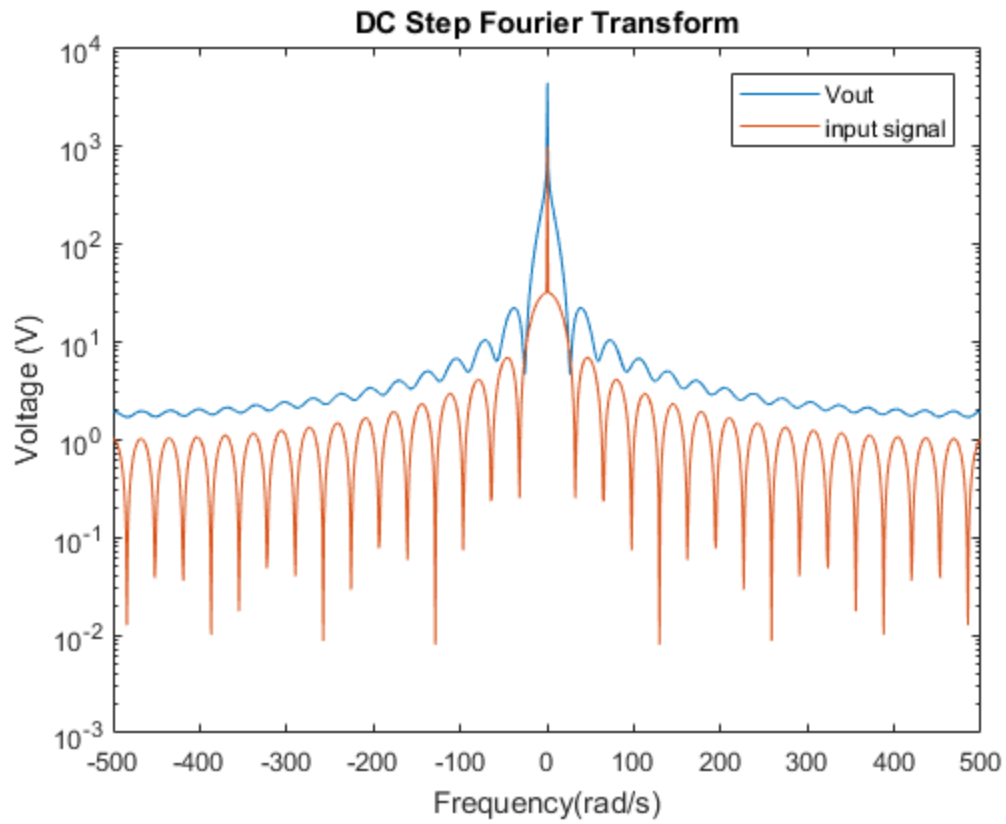

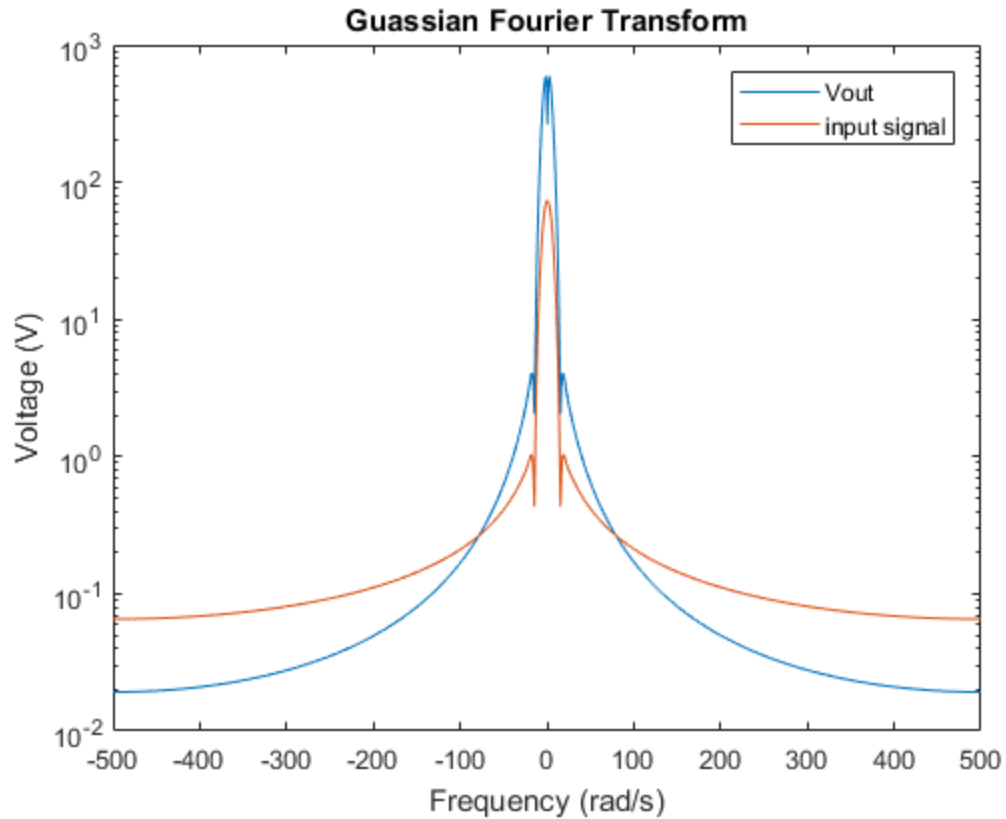

## Question 3

```
iin=0.001*randn();
c2=.00001;

% G matrix
G=[1,0,0,0,0,0,0,0;
   -g2,g1+g2,-1,0,0,0,0,0;
   0,1,0,-1,0,0,0,0;
   0,0,-1,g3,0,0,0,-1;
   0,0,0,0,-a,1,0,0;
   0,0,0,g3,-1,0,0,0;
   0,0,0,0,0,-g4,g4+g5,0;
   0,0,0,0,0,0,0,1];

% C matrix
C=[0,0,0,0,0,0,0,0;
   -c,c,0,0,0,0,0,0;
   0,0,-1,0,0,0,0,0;
   0,0,0,c2,0,0,0,0;
   0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0];
```

---

```

F=[vin;0;0;0;0;0;0;0;iin];

v3=0;
t = linspace(0,1,1000);
dt=0.001;
f=1/.03;
F3=0;

for i=1:1000
    iin=0.001*randn();
    F3(i,1:8)=[exp(-1/2*((t(i)-0.06)/0.03)^2),0,0,0,0,0,0,iin];
end

v3(1:8,1)=(C/dt+G)^-1 *(F3(1,:))';
for i=2:1000
    v3(:,i)=(C/dt+G)^-1 *(C*v3(:,i-1)/dt+F3(i,:))';
end

figure(13)
plot(t,v3(7,:))
hold on
plot(t,F3(:,1))
title('Plot of gaussian source with noise')
legend('Vout','input signal')
xlabel('Time (s)')
ylabel('Voltage (V)')

figure(14)
semilogy(linspace(-500,500,1000),fftshift(abs(fft(v3(7,:)))))
hold on
semilogy(linspace(-500,500,1000),fftshift(abs(fft(F3(:,1)))))
title('Gaussian Fourier Transform with Noise')
legend('Vout','input signal')
xlabel('Frequency (rad/s)')
ylabel('Voltage (V)')

% change the c value
c2=.00002;
C=[0,0,0,0,0,0,0,0;
    -c,c,0,0,0,0,0,0;
    0,0,-1,0,0,0,0,0;
    0,0,0,c2,0,0,0,0;
    0,0,0,0,0,0,0,0;
    0,0,0,0,0,0,0,0;
    0,0,0,0,0,0,0,0;
    0,0,0,0,0,0,0,0];

v3=0;
v3(1:8,1)=(C/dt+G)^-1 *(F3(1,:))';
for i=2:1000
    v3(:,i)=(C/dt+G)^-1 *(C*v3(:,i-1)/dt+F3(i,:))';
end

figure(15)

```

---

---

```

plot(t,v3(7,:))
hold on
plot(t,F3(:,1))
title('Plot of guassian source with cn=0.00002')
legend('Vout','input signal')
xlabel('Time (s)')
ylabel('Voltage (V)')

c2=.0002;
C=[0,0,0,0,0,0,0,0,0;
   -c,c,0,0,0,0,0,0,0;
   0,0,-1,0,0,0,0,0,0;
   0,0,0,c2,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0];

v3=0;
v3(1:8,1)=(C/dt+G)^-1 *(F3(1,:))';
for i=2:1000
    v3(:,i)=(C/dt+G)^-1 *(C*v3(:,i-1)/dt+F3(i,:))';
end

figure(16)
plot(t,v3(7,:))
hold on
plot(t,F3(:,1))
title('Plot of guassian source with cn=0.0002')
legend('Vout','input signal')
xlabel('Time (s)')
ylabel('Voltage (V)')

c2=.002;
C=[0,0,0,0,0,0,0,0,0;
   -c,c,0,0,0,0,0,0,0;
   0,0,-1,0,0,0,0,0,0;
   0,0,0,c2,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0,0];

v3=0;
v3(1:8,1)=(C/dt+G)^-1 *(F3(1,:))';
for i=2:1000
    v3(:,i)=(C/dt+G)^-1 *(C*v3(:,i-1)/dt+F3(i,:))';
end

figure(17)
plot(t,v3(7,:))
hold on
plot(t,F3(:,1))
title('Plot of guassian source with cn=0.002')

```

---

---

```

legend('Vout','input signal')
xlabel('Time (s)')
ylabel('Voltage (V)')

% Decreasing the capacitor increases the noise in the output. As the
% capacitor value is increased to 0.002, the noise decreases until it
can
% not be seen.

c2=.00001;
C=[0,0,0,0,0,0,0,0;
   -c,c,0,0,0,0,0,0;
   0,0,-1,0,0,0,0,0;
   0,0,0,c2,0,0,0,0;
   0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0;
   0,0,0,0,0,0,0,0];

% different time step

v3=0;
t = linspace(0,1,750);
dt=0.0013;
f=1/.03;
F3=0;
for i=1:750
    iin=0.001*randn();
    F3(i,1:8)=[exp(-1/2*((t(i)-0.06)/0.03)^2),0,0,0,0,0,0,iin];
end

v3(1:8,1)=(C/dt+G)^-1 *(F3(1,:)');
for i=2:750
    v3(:,i)=(C/dt+G)^-1 *(C*v3(:,i-1)/dt+F3(i,:)');
end

figure(18)
plot(t,v3(7,:))
hold on
plot(t,F3(:,1))
title('Plot of gaussian source with noise with dt =.0013 ')
legend('Vout','input signal')
xlabel('Time (s)')
ylabel('Voltage (V)')

v3=0;
t = linspace(0,1,500);
dt=0.2;
f=1/.03;
F3=0;
for i=1:500
    iin=0.001*randn();

```

---



---

```


    F3(i,1:8)=[exp(-1/2*((t(i)-0.06)/0.03)^2),0,0,0,0,0,0,iin];
end



v3(1:8,1)=(C/dt+G)^-1 *(F3(1,:))';
for i=2:500
    v3(:,i)=(C/dt+G)^-1 *(C*v3(:,i-1)/dt+F3(i,:))';
end



figure(19)
plot(t,v3(7,:))
hold on
plot(t,F3(:,1))
title('Plot of gaussian source with noise and dt=0.2')
legend('Vout','input signal')
xlabel('Time (s)')
ylabel('Voltage (V)')



% When the time step is increased, we see the shape of the output
% change.
% At higher time steps, the area of the gaussian which goes below 0V
% disappears. The plots are also less noisy than the plots with lower
% time
% steps

```

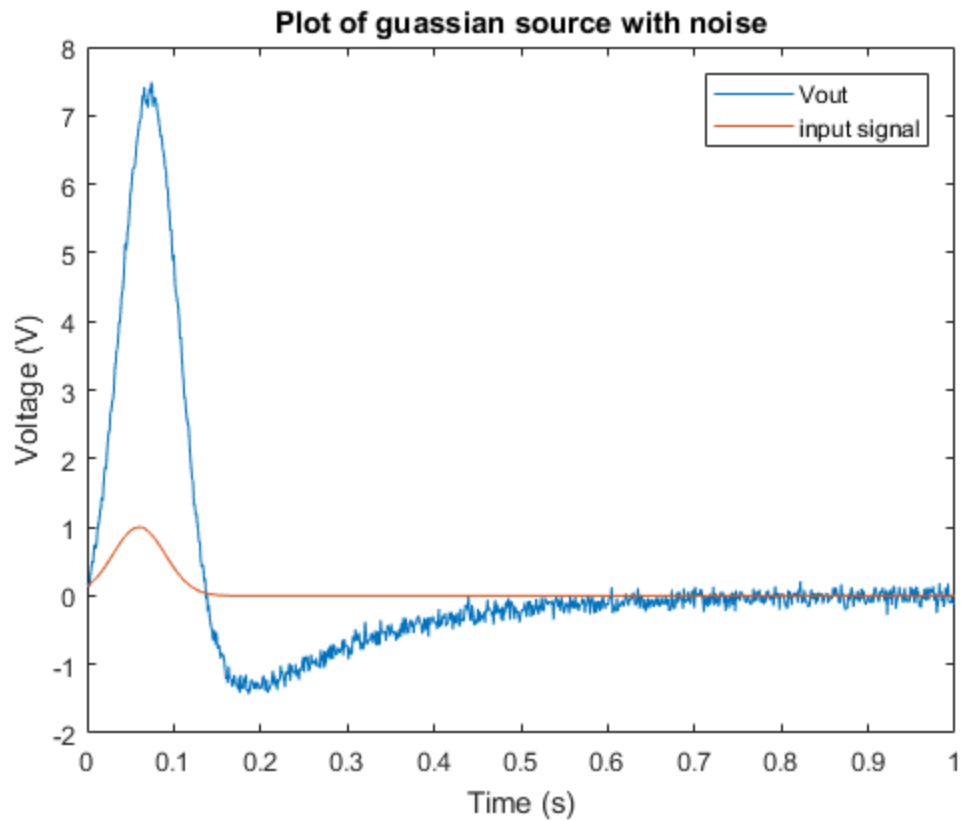

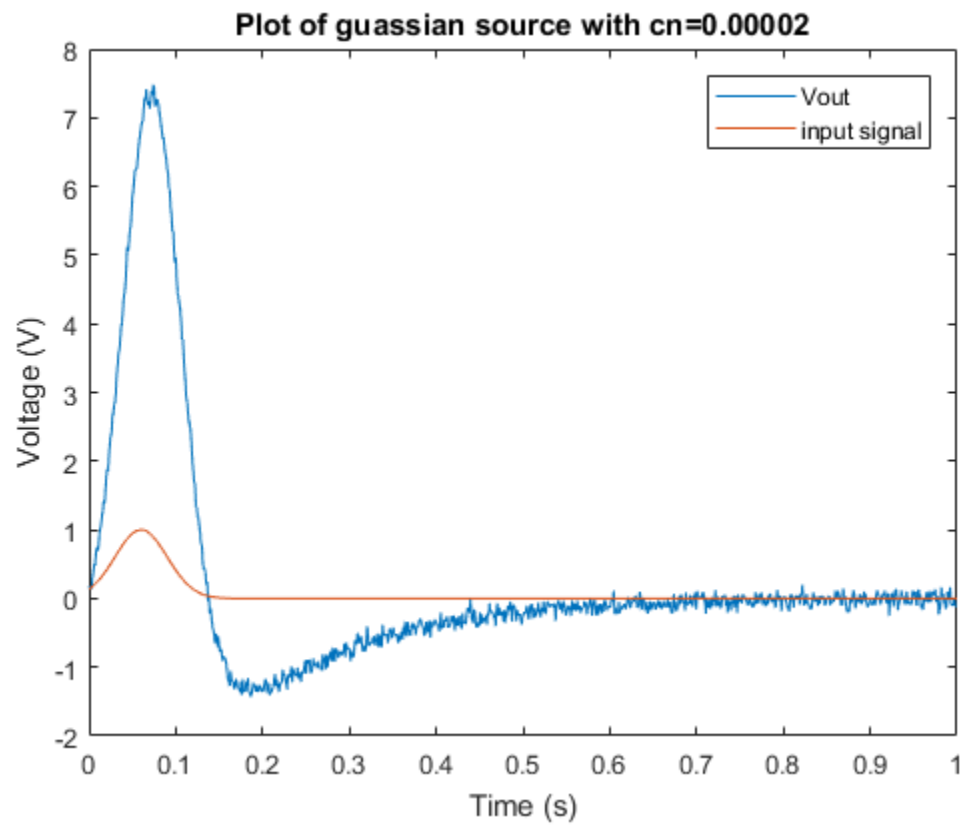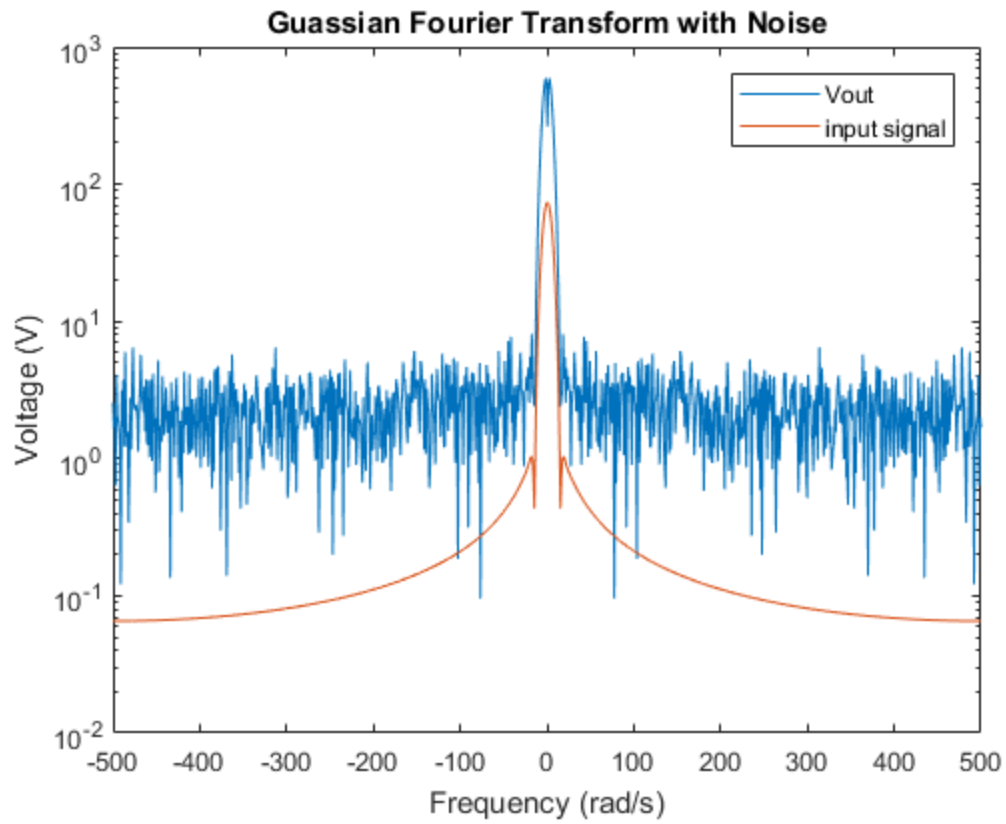

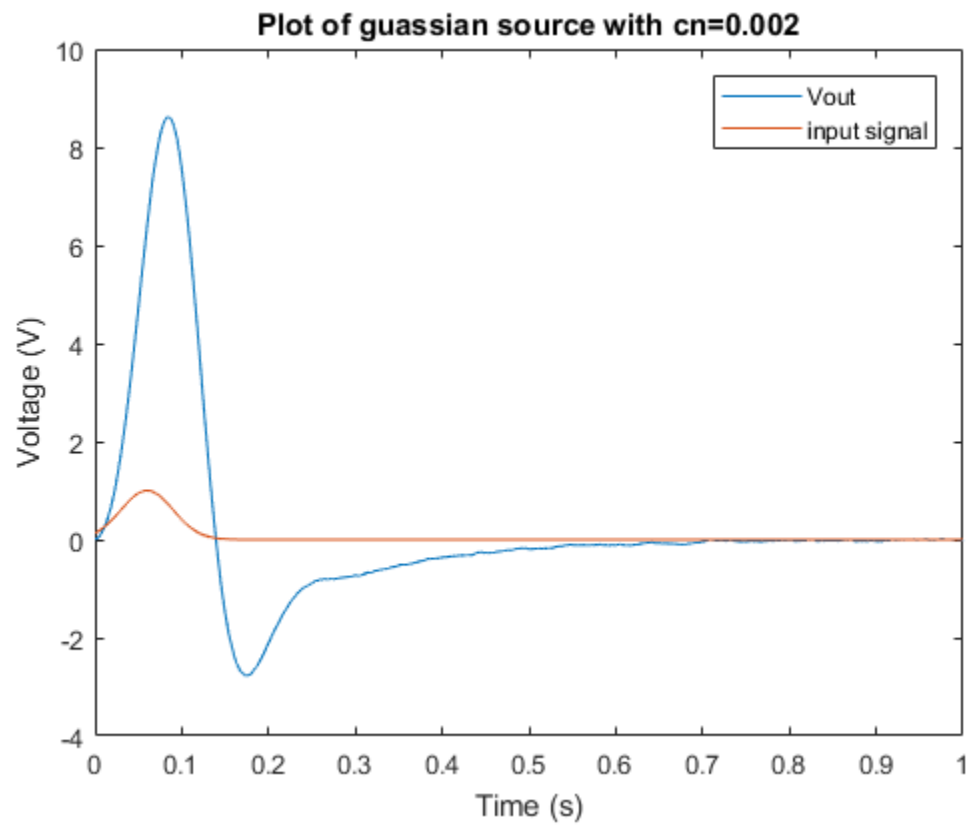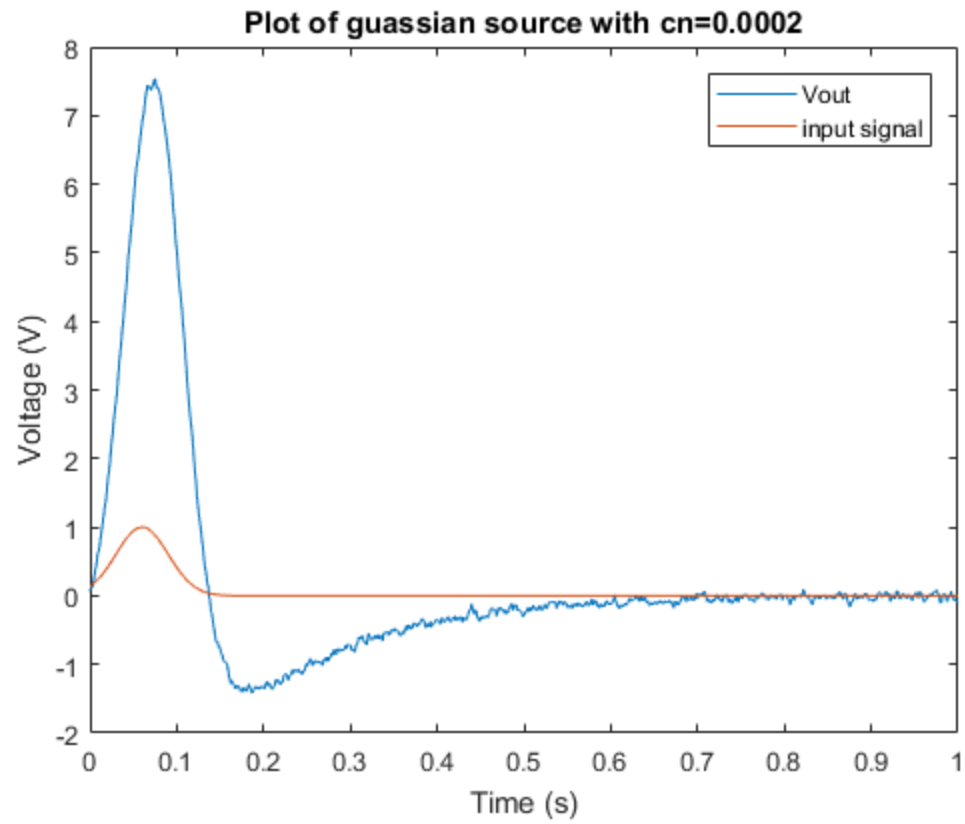

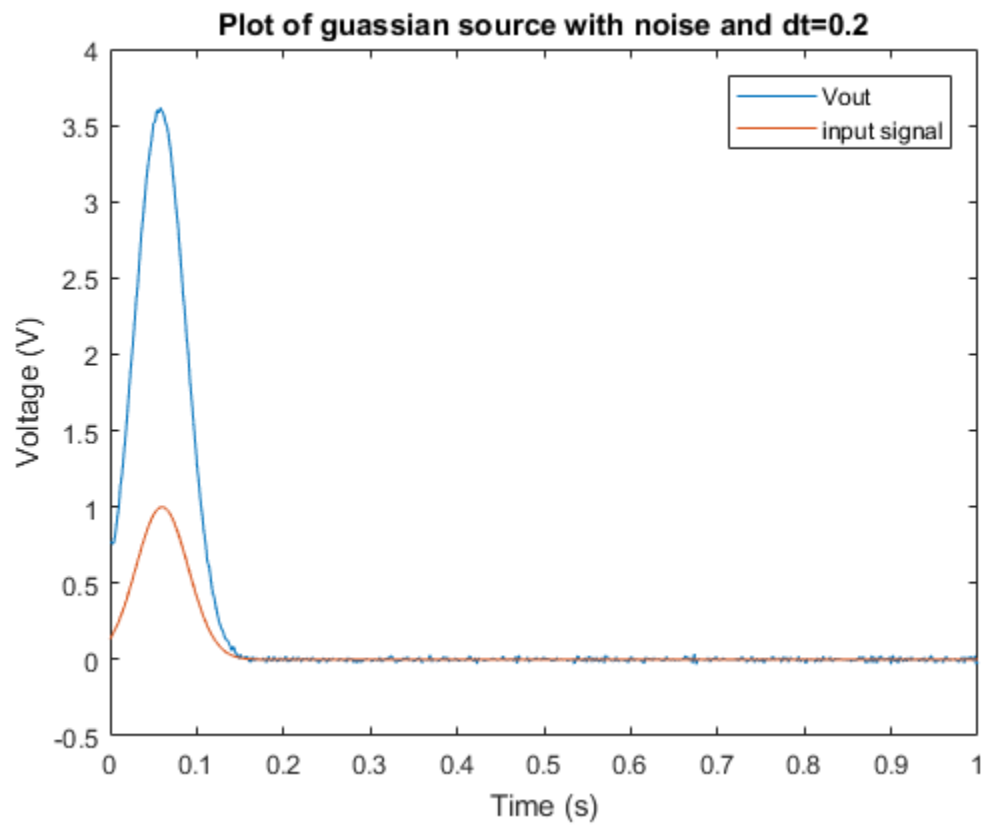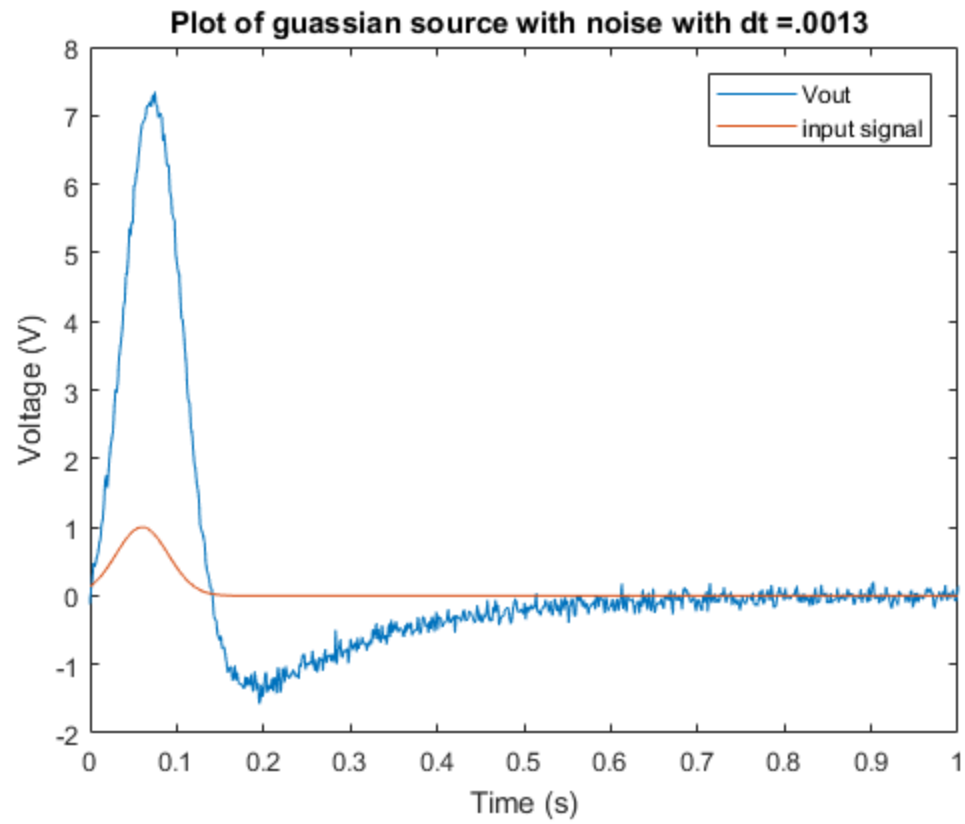

---

## Question 4

In order to implement the non linearity, introduce a new matrix for the non linear components. With the new matrix, the equation to solve for V must be include the extra b matrix added to GX. to create the B matrix, have a matrix where the V4 component is  $\beta * (V_3 * G_3)^2 + \gamma(V_3 * G_3)^3$  the new equation is:

$C \frac{dV}{dt} + GV + B = F$  in order to do this we need to do a newton iteration at every step to make sure Vj converges at every time step.

*Published with MATLAB® R2017a*